

[Type here]

INDEX

S. No	Content
01	Implementation and Design of NAND gate using DSCH03
02	Relationship of NAND gate using μ -wind
03	Design and logic verification of combine circuit of $Y = \overline{AB} + \overline{CD}$ using μ -wine.
04	Observation and verification of transfer characteristics of CMOS inverter.
05	Implementation and Design of full adder circuit using ASIC design tools. $Y = A \oplus B \oplus C$ and Carry = $AB + BC + CA$
06	Verification of nMOS and pMOS DC-Characteristics